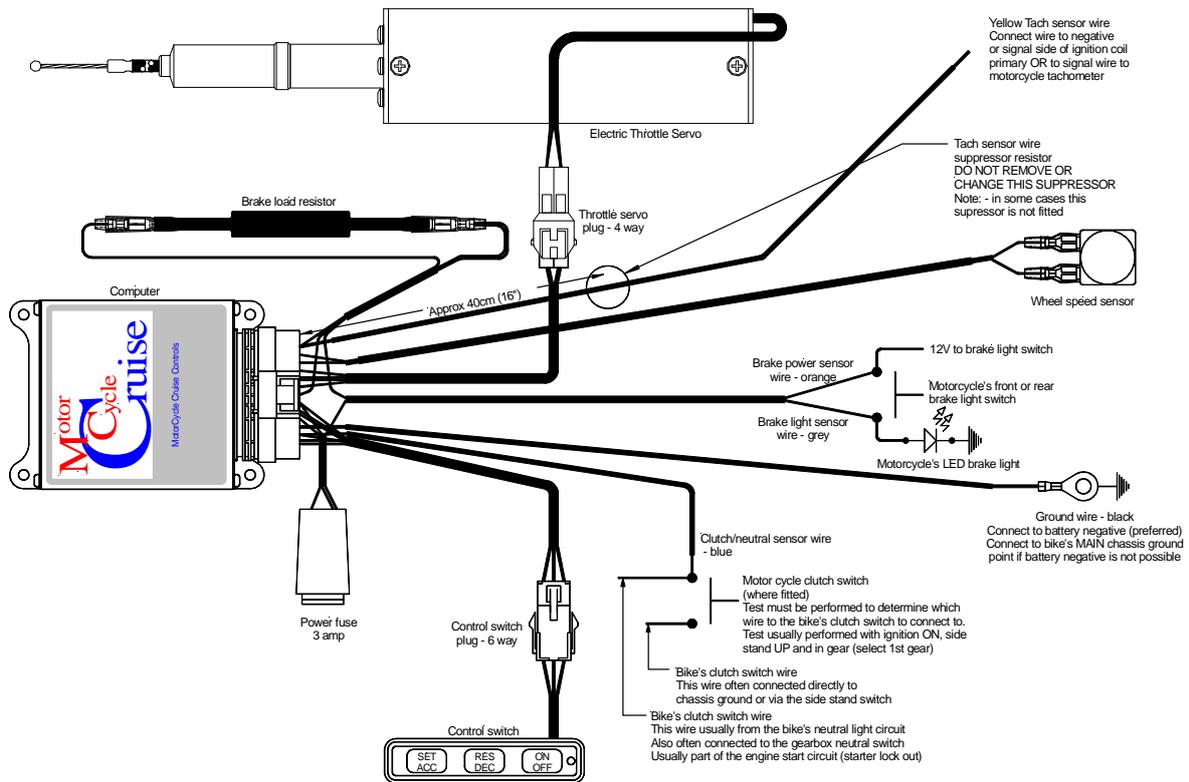


Installing the wiring harness.

The following diagram shows the basic connections required for the cruise control.



The following instructions show the connections to be made in detail.

Connect the large connector to the cruise control computer (right arrow).

Separate the brake load resistor branch from the other branches of the harness. This branch is a rectangular resistor covered in heat shrink tube with bullet terminals on the ends (see next photo).

Route all the other branches of the main cruise control harness from the computer forward between the battery and the fuse box.

